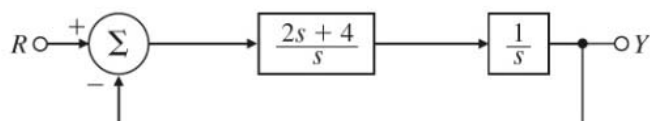


# ESE 406/505 & MEAM 513 – 2011-Feb-07 – Quiz – Name: \_\_\_\_\_

- Choose only one answer for each question by circling the letter.
- A correct answer is worth 2 points.
- No answer is worth 0 points.
- An incorrect answer is worth -1 point. Random guessing will hurt you.

1. Which of the following is the transfer function corresponding to the figure at right?




- A.  $\frac{Y(s)}{R(s)} = \frac{2s + 4}{s^2 + 2s + 4}$
- B.  $\frac{Y(s)}{R(s)} = \frac{s^2 - 2s - 4}{s^2}$
- C.  $\frac{Y(s)}{R(s)} = \frac{2s + 4}{s^2}$
- D. None of the above.
2. Which of the following is the correct transfer function for  $\tau \frac{dy}{dt} + 2y = \tau \frac{du}{dt}$ ?

- A.  $\frac{Y(s)}{U(s)} = \frac{\tau s}{\tau s + 2}$
- B.  $\frac{Y(s)}{U(s)} = \frac{\tau}{\tau + 2s}$
- C.  $\frac{Y(s)}{U(s)} = \frac{\tau}{\tau + 2}$
- D. It depends on the initial values of y and u.
3. The effective resistance of two resistors connected in series is...
- A. ...the sum of the resistances.
- B. ...the product of the resistances divided by the sum of the resistances.
- C. ...the difference between the larger and smaller resistance.
- D. ...None of the above.

4. Which of the following is the correct transfer function for the circuit shown below?

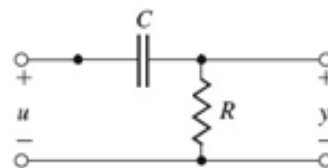- A.  $\frac{Y(s)}{U(s)} = \frac{Cs}{Cs + R}$
- B.  $\frac{Y(s)}{U(s)} = \frac{R}{Cs + R}$
- C.  $\frac{Y(s)}{U(s)} = \frac{1}{RCs + 1}$
- D. None of the above.



5. Which ONE of the following is NOT correct concerning assumptions we made to achieve our description of an "ideal" operational amplifier?
- A. Infinite input impedance  $\rightarrow$  zero current on the inputs.
- B. Infinite output impedance  $\rightarrow$  zero current on the output.
- C. Infinite gain  $\rightarrow$  zero voltage difference between the inputs.