

7 relate $K_c \left(\frac{1.5/2}{1.5/10} \right)$ to R_1, R_2, τ, L in the circuit
 \downarrow simplifies to

$$K_c \left(\frac{z+s}{z} + \frac{p}{p+s} \right) =$$

looks like a voltage divider

$$p = R_2 \quad s = R_1$$

$$z = \frac{1}{C} \text{ then we get } 1 + RC \leftarrow \tau \text{ for filter}$$

8

mag lev system w/ sensor

$$f(I_0, \gamma_0) + K_c i + K_x x - mg = K_i i + K_x x$$

Desired position looks like a differential amplifier
 out and offset

$$\frac{dV}{dt} = \frac{R_1 + R_2}{R_1} + \frac{dR}{dt} \frac{dI}{dt} - \frac{R_2}{R_1} \frac{dI}{dt}$$

variable resistor

Current offset circuit
 inverting amplifier

$$V_{in}(t) - V_-(t) = i(t) R_{in}$$

$$V_{out} = \frac{10K}{R_3} V_{in} = \frac{10K + \frac{dR}{dt} + R_3}{dR}$$

$$V_o(t) = \frac{10K (20K + \frac{dR}{dt})}{R_3} V_i(t)$$

variable resistor